

1. What is the value of a capacitor with 250 volts applied having 750 pC of charge?

$$Q = CV$$

$$\therefore C = \frac{Q}{V} = \frac{750 \text{ pC}}{250 \text{ V}} = \boxed{3.0 \text{ pF}}$$


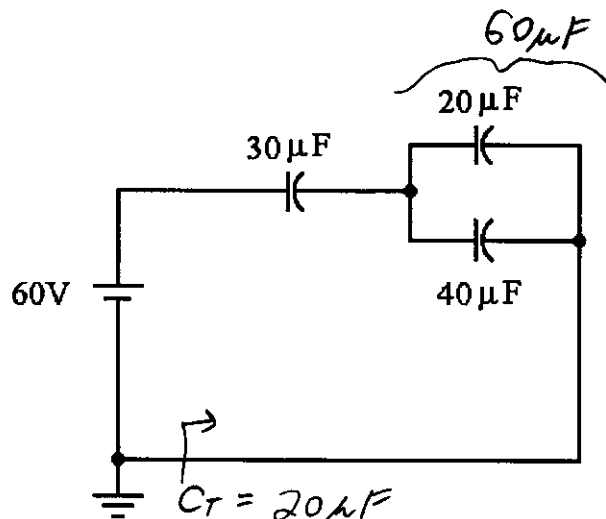



Figure 10.6

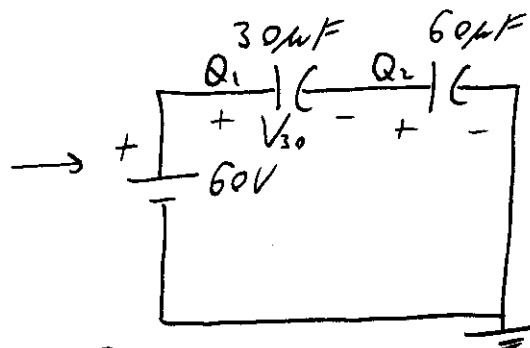

$$Q_T = Q_1 = Q_2 \\ = (20 \mu\text{F})(60\text{V}) = \underline{1.2 \text{ mC}}$$

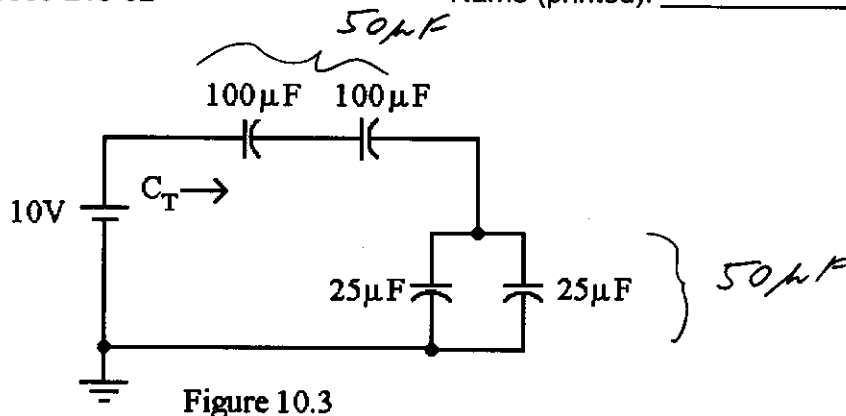
2. See Figure 10.6. What is the voltage across the 30 μF capacitor?

$$V_{30} = \frac{Q_{30}}{30 \mu\text{F}} = \frac{1.2 \text{ mC}}{30 \mu\text{F}} = \boxed{40 \text{ V}}$$



3. See Figure 10.3. What is the total capacitance C_T ?

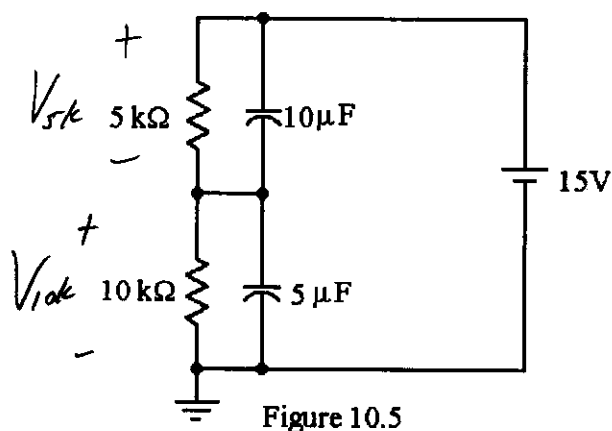- a. 12.5 μF
- b. 25 μF
- c. 50 μF
- d. 212.5 μF



$$V_{5k} = 15V \left(\frac{5k\Omega}{5k\Omega + 10k\Omega} \right) = \underline{\underline{5V}}$$

$$V_{10k} = 15V \left(\frac{10k\Omega}{10k\Omega + 5k\Omega} \right) = \underline{\underline{10V}}$$

$C \rightarrow \infty$
AFTER
CHARGED

4. See Figure 10.5. What is the voltage across the 5 μF capacitor after each capacitor has charged to its final value?

- a. 0 V
- b. 5 V
- c. 10 V
- d. 15 V

5. See Figure 10.5. What is the voltage across the 10 μF capacitor after each capacitor has charged to its final value?

- a. 0 V
- b. 15 V
- c. 10 V
- d. 5 V