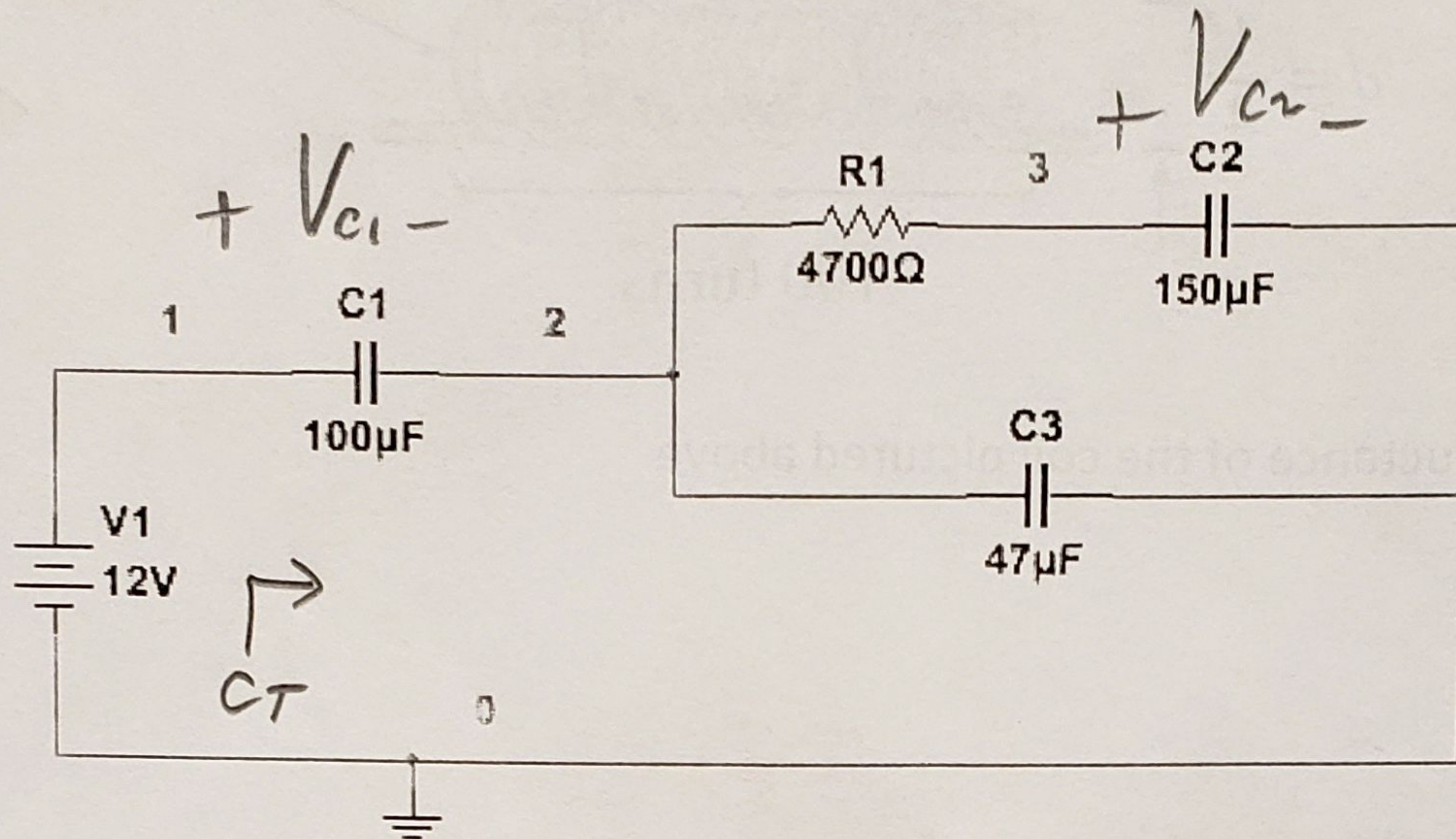


NAME (first and last): * SOLUTIONS *

Section: _____


All 5 questions are equally weighted, circle or box-in your final answers. No partial credit will be awarded, choose carefully and check your work:



For the circuit shown above under steady-state conditions:

1. Find the total capacitance seen by source V1 (C_T)

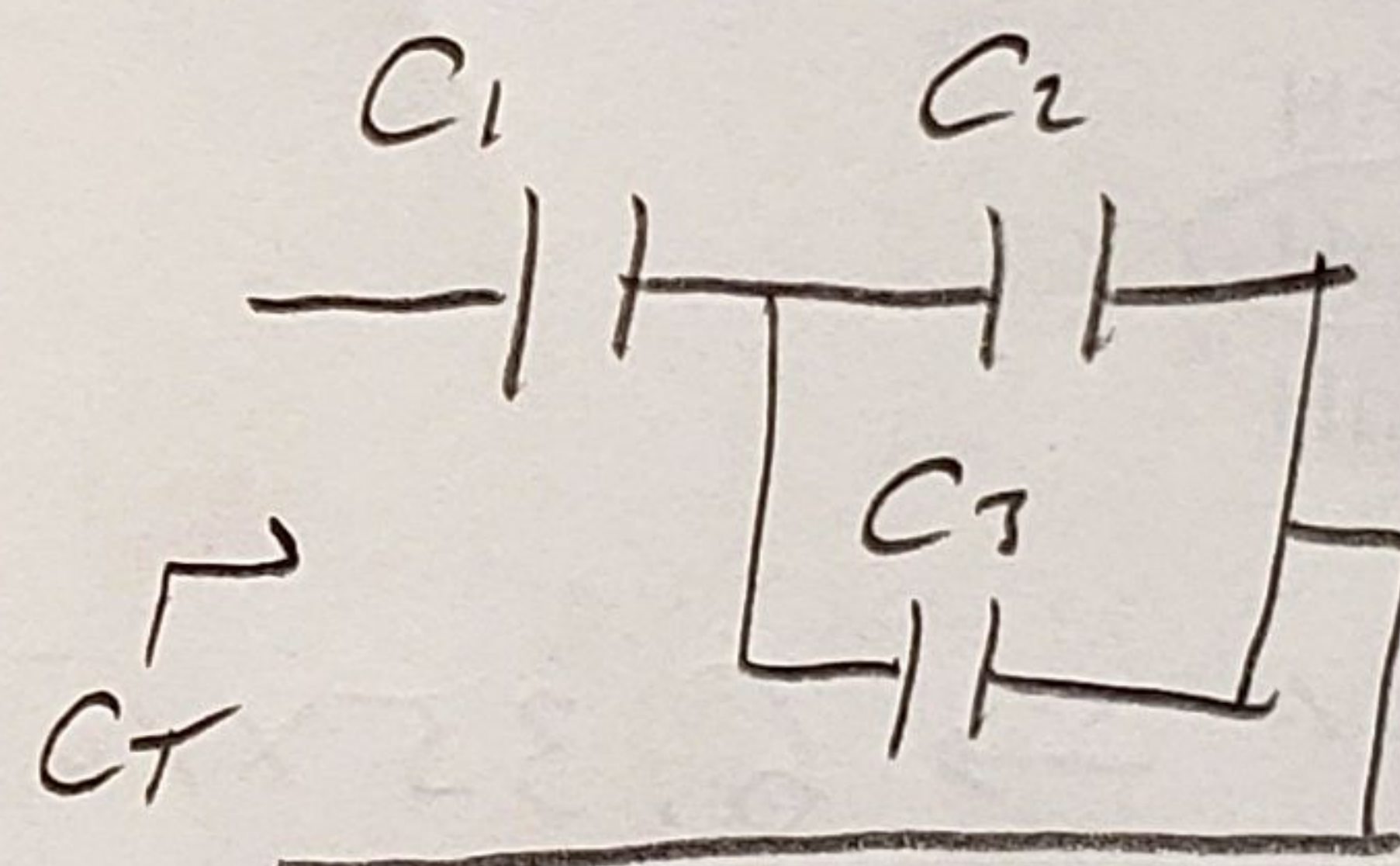- a. 33.6 μF
- b. 66.3 μF
- c. 147 μF
- d. 297 μF



C_1 SERIES WITH $C_2 // C_3$

100 μF SERIES 197 μF

$$C_T = \frac{1}{\frac{1}{100\mu\text{F}} + \frac{1}{197\mu\text{F}}} = 66.3\mu\text{F}$$

2. Find the total charge on C_T

- a. 40.4 μC
- b. 190 μC
- c. 606 μC
- d. 796 μC

$$Q = CV$$

$$= (66.3\mu\text{F})(12\text{V})$$

$$= 796\mu\text{C}$$

3. Find the voltage across C_2

- a. 4.0 V
- b. 6.1 V
- c. 8.0 V
- d. 12 V

$$Q_{C1} = Q_T \text{ (IN SERIES)}$$

$$Q_{C1} = (V_{C1})(C_1)$$

$$\text{OR } V_{C1} = \frac{Q_{C1}}{C_1} = \frac{796\mu\text{C}}{100\mu\text{F}} = 7.96\text{V}$$

Questions 4 & 5 on the back →


HENCE

$$V_{C2} = V_{C3} = V_1 - V_{C1}$$

$$= 4.04\text{V}$$

$$L = \frac{N^2 \mu_r \mu_0 A}{l}$$

$$A = \frac{\pi d^2}{4}$$

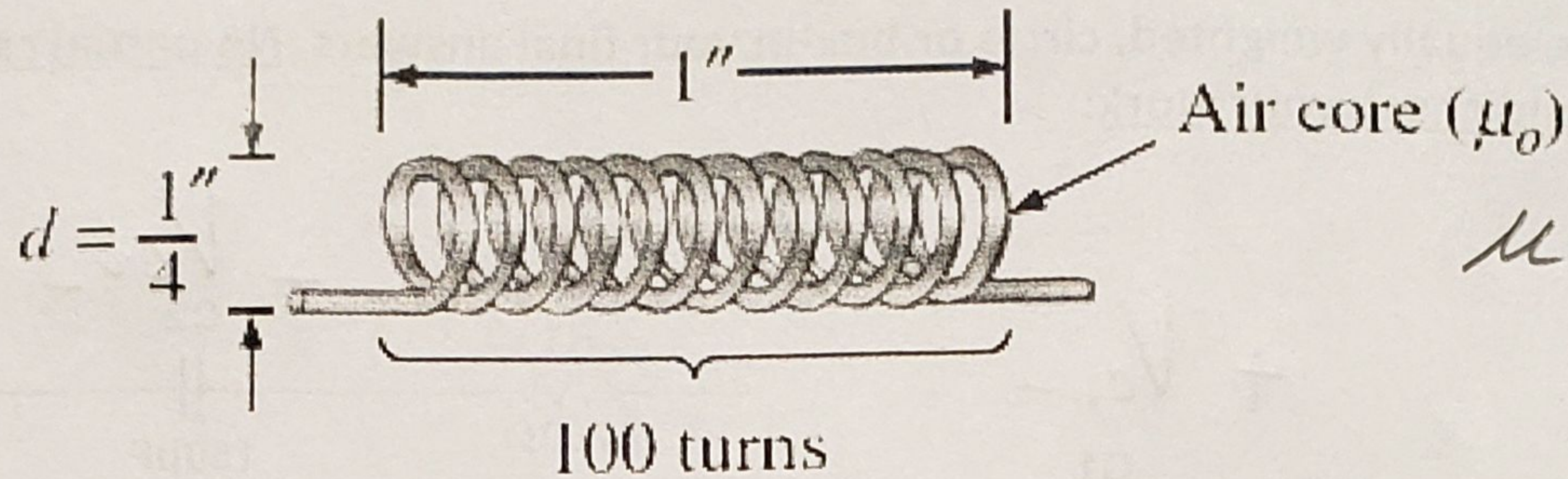

$$\mu_0 = 4\pi \times 10^{-7} \frac{\text{Wb}}{\text{A}\cdot\text{m}}$$

4. Find the inductance of the coil pictured above

- a. 6.35 μH
- b. 15.7 μH
- c. 31.4 μH
- d. 80.0 μH

5. If the air core is replaced by an iron alloy (with $\mu_r = 300$), what would the inductance change to?

- a. 953 μH
- b. 2.35 mH
- c. 4.70 mH
- d. 31.4 mH

$$0.25'' \rightarrow 6.35 \times 10^{-3} \text{ m}$$

$$1'' = 25.4 \text{ mm} \times 10^{-3} \text{ m}$$

$$A = \frac{\pi d^2}{4} = \frac{\pi (6.35 \times 10^{-3} \text{ m})^2}{4} = 31.67 \times 10^{-6} \text{ m}^2$$

$$\therefore L_0 = \frac{(100)^2 \left(4\pi \times 10^{-7} \frac{\text{Wb}}{\text{A}\cdot\text{m}} \right) (31.67 \times 10^{-6} \text{ m}^2)}{25.4 \times 10^{-3} \text{ m}} \quad \left. \vphantom{\frac{(100)^2 \left(4\pi \times 10^{-7} \frac{\text{Wb}}{\text{A}\cdot\text{m}} \right) (31.67 \times 10^{-6} \text{ m}^2)}{25.4 \times 10^{-3} \text{ m}}} \right\} \text{AIR CORE}$$

$$L_0 = 15.67 \mu\text{H}$$

$$L = \mu_r L_0 = (15.67 \mu\text{H}) (300) = 4.70 \text{ mH}$$

\uparrow
 300 (IRON Alloy)