

Figure 7.1

1. See Figure 7.1; what is the total resistance R_T as "seen" by the voltage source?

- a. 2.4 ohms
- ☒ b. 3.2 ohms
- c. 4.8 ohms
- d. 6.4 ohms

$$R_T = 16 // 12 // [6 // 3 + 4] \\ = 6.86 // [2 + 4] = \boxed{3.2 \Omega}$$

2. See Figure 7.1. What is the current through the 6 ohm resistor?

- ☒ a. 0.67 A
- b. 3.00 A
- c. 2.00 A
- d. 1.33 A

$$I_T = \frac{12V}{R_T} = \frac{12V}{3.2 \Omega} = \underline{3.75A}$$

$$I_{4\Omega} = \frac{12V}{6\Omega} = \underline{2A}$$

$$I_{6\Omega} = \underset{\substack{\uparrow \\ I_T}}{2A} \left(\underset{\substack{\uparrow \\ R_x}}{\frac{2\Omega}{6\Omega}} \right) = \boxed{0.66A}$$

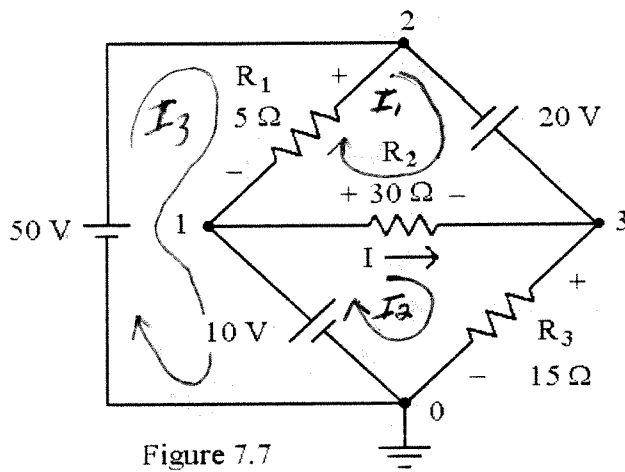


Figure 7.7

3. See Figure 7.7; Find the MESH currents (as assigned above):

- a. $I_1 = 14.67 \text{ A}$, $I_2 = 6.67 \text{ A}$, $I_3 = 4.67 \text{ A}$
- b. $I_1 = 6.67 \text{ A}$, $I_2 = 4.67 \text{ A}$, $I_3 = 14.67 \text{ A}$**
- c. $I_1 = 4.67 \text{ A}$, $I_2 = 14.67 \text{ A}$, $I_3 = 6.67 \text{ A}$
- d. $I_1 = 6.67 \text{ A}$, $I_2 = 14.67 \text{ A}$, $I_3 = 4.67 \text{ A}$

$$\begin{aligned} \textcircled{1} \quad (I_3 - I_1)R_1 + 20 + (I_2 - I_1)R_2 &= 0 \Rightarrow -35I_1 + 30I_2 + 5I_3 = -20 \quad (1) \\ \textcircled{2} \quad 10 + (I_1 - I_2)R_2 - I_2R_3 &= 0 \Rightarrow 30I_1 - 45I_2 + 0I_3 = -10 \quad (2) \\ \textcircled{3} \quad 50 + (I_1 - I_3)R_1 - 10 &= 0 \Rightarrow 5I_1 + 0I_2 - 5I_3 = -40 \quad (3) \end{aligned}$$

SOLVING YIELDS:

$$I_1 = 6.67 \text{ A}$$

$$I_2 = 4.67 \text{ A}$$

$$I_3 = 14.67 \text{ A}$$

4. See Figure 7.7; Determine "I," the current through R_2 (in the direction shown):

- a. -2.0 A**
- b. 2.0 A
- c. 10.0 A
- d. -10.0 A

$$I_{R_2} = I_2 - I_1 = \boxed{-2 \text{ A}}$$

5. See Figure 7.7; Determine the power dissipated by R_1 .

- a. 327 W
- b. 320 W**
- c. 246 W
- d. 60.0 W

$$P_{R_1} = (I_3 - I_1)^2 R_1 = \boxed{320 \text{ W}}$$

6. See Figure 7.7; Determine the current flowing through R_3 .

- a. 4.67 A, down**
- b. 8 A, down
- c. 4.67 A, up
- d. 6.67 A, down

$$I_2 \Rightarrow \boxed{4.67 \text{ A, DOWN}}$$

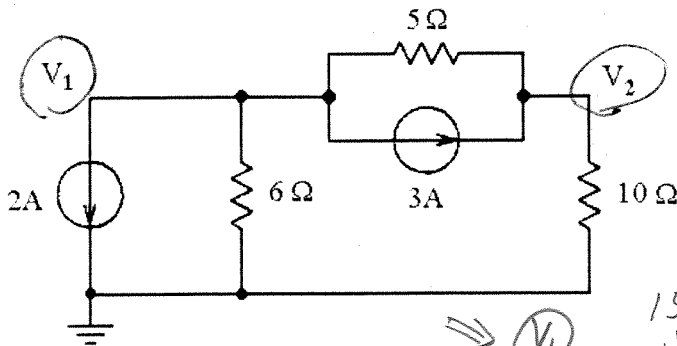




Figure 8.7

7. See Figure 8.7. Find V_1 and V_2

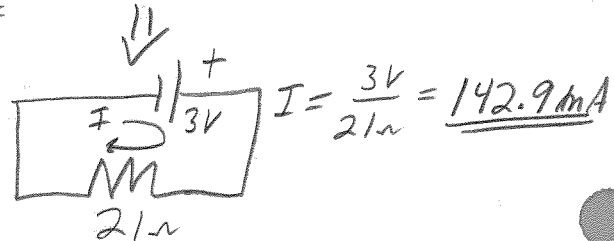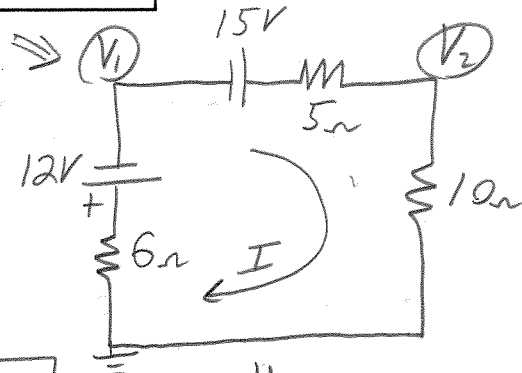- a. $V_1 = -24 \text{ V}$, $V_2 = 30 \text{ V}$
- ☒ b. $V_1 = -12.9 \text{ V}$, $V_2 = 1.43 \text{ V}$
- c. $V_1 = -8.01 \text{ V}$, $V_2 = 4.66 \text{ V}$
- d. $V_1 = -1.43 \text{ V}$, $V_2 = -17.6 \text{ V}$

KVL: $V_1 = -12\text{V} - I(6\Omega) = \boxed{-12.86\text{V}}$

KVL: $V_2 = I(10\Omega) = \boxed{1.429\text{V}}$



8. See Figure 8.7. Find the current through the 5 ohm resistor:


- a. 10.8 A, right to left
- b. 0.67 A, left to right
- ☒ c. 2.86 A right to left
- d. 3.23 A, left to right



$$I_{5\Omega} = \frac{V_2 - V_1}{5\Omega} = \frac{14.29\text{V}}{5\Omega} = \boxed{2.86\text{A}}$$

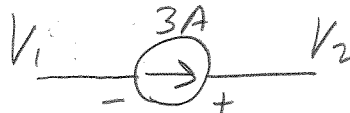9. See Figure 8.7. Find the power delivered by the 3A source:

- ☒ a. 42.9 W
- b. 162 W
- c. 38.0 W
- d. 48.5 W




$$P_{3A} = I(V_2 - V_1)$$

$$= 3\text{A}(14.29\text{V})$$

$$\boxed{P_{3A} = 42.87\text{W}}$$

Figure 5.70

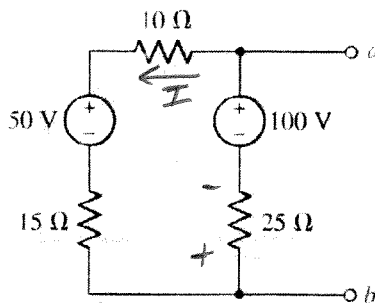

$$R_{TH} = (10 + 15) // 25$$

$$R_{TH} = 12.5 \Omega$$

$$V_{TH} = 100V - 25\Omega(I)$$

$$I = \frac{100V - 50V}{50\Omega} = 1A$$

$$V_{TH} = 100 - 25 = 75V$$

10. For Figure 5.70: Find the Thevenin equivalent resistance (R_{TH}) looking back into the circuit from terminals a-b (the load has already been removed):


a. 50 ohms
b. 12.5 ohms
 c. 25 ohms
 d. 0 ohms

11. For Figure 5.70: Find the Thevenin equivalent voltage (V_{TH}) looking back into the circuit from terminals a-b (the load has already been removed):

a. 150 V
 b. 37.5 V
c. 75 V
 d. 50 V

12. See Figure 5.70. How much power would be delivered to a 12.5-ohm resistor placed between terminals a-b?

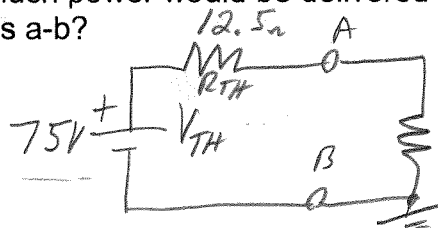a. 113 W
 b. 44.4 W
 c. 38.5 W
 d. 67.9 W



$$I = \frac{75V}{25\Omega} = 3A$$

$$P = I^2 \cdot R = 112.5W$$

13. See Figure 5.70. How much power would be delivered to a 100-ohm resistor placed between terminals a-b?

a. 44.4 W
 b. 64.2 W
 c. 62.1 W
 d. 38.5 W

w/ 100Ω LOAD

$$I = \frac{75V}{112.5\Omega} = 666.7mA$$

$$P = I^2 \cdot R = 44.44W$$


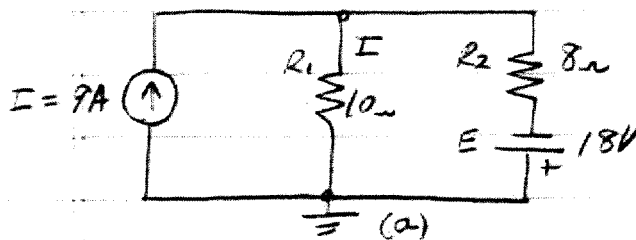



Figure 2 – Circuit for Problems 14 and 15

14. See Figure 2 above. Find the current that flows through R_1 due only to the 18V source and the direction of this current:
- 4 A, top to bottom
 - 2.23 A, bottom to top
 - 5 A, top to bottom
 - ☒ 1 A, bottom to top
15. See Figure 2 above. Find the total current that flows through R_1 and the direction of this current:
- ☒ 3 A, top to bottom
 - 2.23 A, bottom to top
 - 1 A, top to bottom
 - 6.77 A, top to bottom

DUE TO 18V

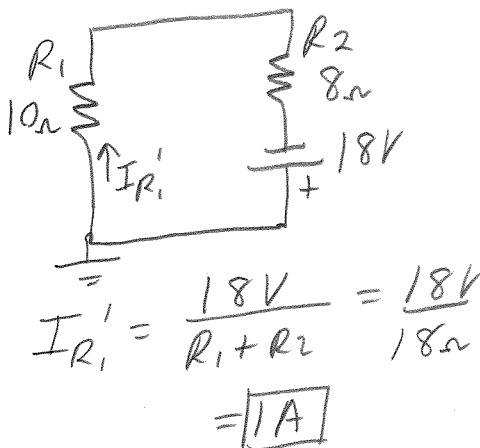

DUE TO I

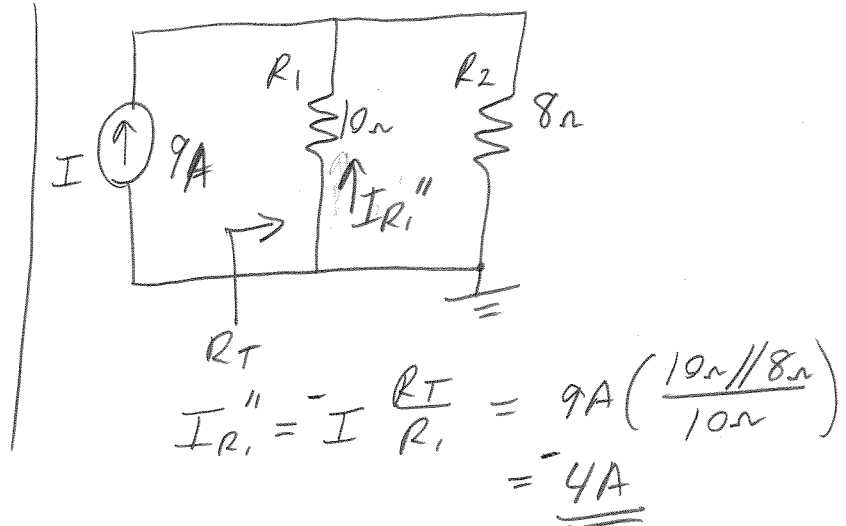

$$\therefore I_{R_1} = 1 - 4 = \boxed{-3A} \text{ Bottom To Top}$$

OR 3A Top To Bottom