

TEAM NAME (printed): * SOLUTIONS *

Team members PRESENT (printed names):

MULTIPLE CHOICE: Circle the one alternative that best completes the statement or answers the question. No partial credit will be awarded

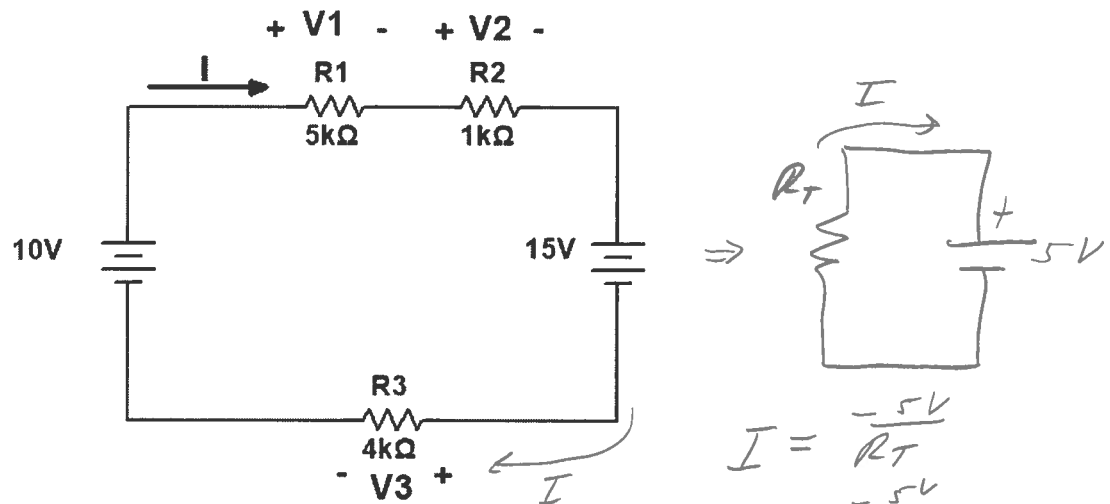


Figure 1

1) See Figure 1. Which one of the following KVL equations describes this circuit?

A) $+10\text{ V} - V_1 - V_2 - 15\text{ V} - V_3 = 0$ ✓

C) $-10\text{ V} - V_1 - V_2 - 15\text{ V} - V_3 = 0$ ✗ ✗ ✗ ✗

B) $+10\text{ V} - V_1 - V_2 + 15\text{ V} - V_3 = 0$ ✗

D) $+10\text{ V} + V_1 + V_2 - 15\text{ V} + V_3 = 0$ ✗ ✗ ✗

2) See Figure 1. The total current I is:

A) $-500\text{ }\mu\text{A}$ ✓

B) $+2.5\text{ mA}$

C) $+500\text{ }\mu\text{A}$

D) -2.5 mA

3) See Figure 1. Voltage V3 is:

A) 10 V

B) -10 V

C) 5.0 V

D) -2.0 V ✓

Questions 4,5
 →

$$\begin{aligned} V_3 &= I \cdot R_3 \\ &= (-500\text{ }\mu\text{A})(4\text{ k}\Omega) \\ &= \underline{\underline{-2\text{ V}}} \end{aligned}$$


DC Circuits (EEET 111 03)

TEAM Quiz 2181

Series and Voltage Sources


Answer the following questions. Show your work and box-in your final answer. Partial credit may be awarded.

- 4) A series circuit with a voltage source of 15 volts and a total resistance of 7500 ohms will dissipate how much power?



$$P_{RT} = \frac{V_{RT}^2}{R_T} = \frac{(15V)^2}{7500\Omega} = \boxed{30mW}$$

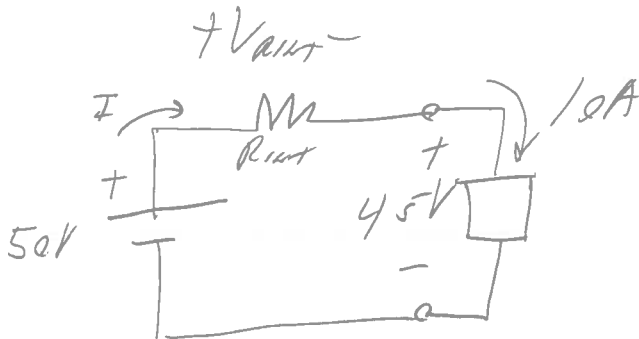- 5) Calculate the internal resistance of a DC power supply if the no-load output voltage is $V_{NL} = 50V$, and the output voltage is 45V with a 10A load is connected.



$$V_{INT} = 5V$$

$$I = 10A$$

$$\therefore R_{INT} = \frac{V_{INT}}{I} = \frac{5V}{10A} = \boxed{0.5\Omega}$$