

FULL NAME (Printed):

\* SOLUTIONS \*

Program: \_\_\_\_\_

You have the entire period to complete this examination. You are allowed your Sharp EL-516 calculator and the DC Formula Sheet from the text (provided). All of the questions are equally weighted

- **M/C Questions**

- ☐ Circle the correct answer
- ☐ NO partial credit will be awarded

- **Work the Problem Questions**

- ☐ SHOW ALL your work in the space provided
  - ☐ BOX-IN your final answer
  - ☐ Partial credit may be awarded
-

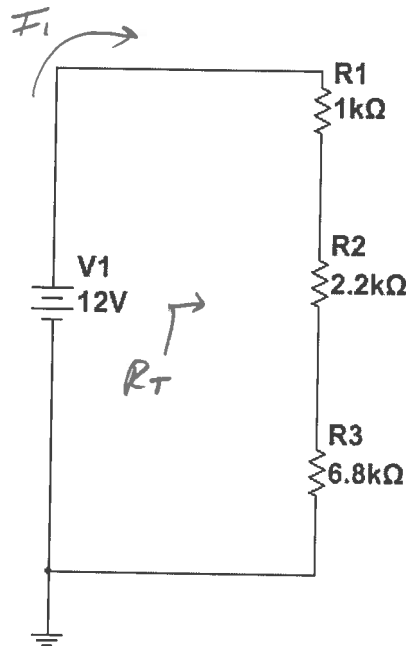


Figure 1 - Schematic for Problems 1 - 3

1. See Figure 1. The total resistance in this circuit is (as seen by the source):

a. 624 Ohms  
 b. 1000 Ohms  
 c. 10 k-Ohms  
 d. 12 k-Ohms

$$R_T = R_1 + R_2 + R_3 = 10k\Omega$$

2. See Figure 1. The total current flowing from the battery is


a. 1.0 mA  
 b. 1.2 mA  
 c. 1.8 mA  
 d. 12 mA

$$I_1 = \frac{V_1}{R_T} = \frac{12V}{10k\Omega} = 1.2mA$$

3. See Figure 1. The total power dissipated by the 2.2 k-ohm resistor is

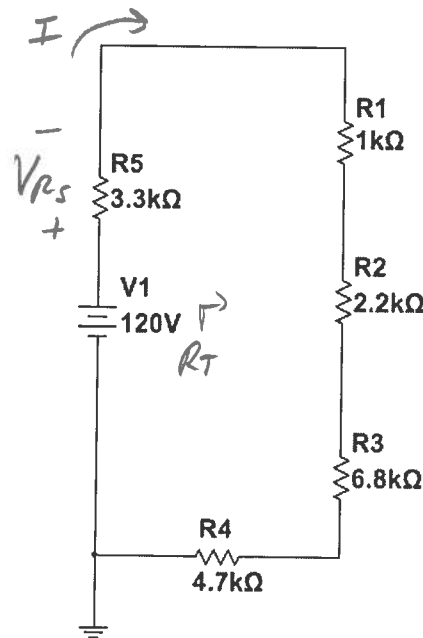a. 3.17 mW  
 b. 14.4 mW  
 c. 23.2 mW  
 d. 144 mW

$$P_{R_2} = (I_{R_2})^2 R_2 = (I_1)^2 R_2 = (1.2mA)^2 (2200\Omega) = 3.17mW$$



$$R_T = R_1 + R_2 + R_3 + R_4 + R_5$$

$$= 18k\Omega$$

Figure 2- Schematic for Problems 4 through 6

4. See Figure 2. How much power is dissipated by R5?

a. 6.67 mW  
b. 36.4 mW  
c. 132.2 mW  
d. 146.7 mW

$$P_{R5} = \frac{V_{R5}^2}{R5}, \quad V_{R5} = V_1 \frac{R5}{R_T}$$

$$= 120V \left( \frac{3.3k\Omega}{18k\Omega} \right)$$

$$= 22V$$

5. See Figure 2. If R3 is open circuited, how much power is dissipated by R5?

a. 0 W  
b. 1.76 mW  
c. 6.76 mW  
d. 36.4 mW

$$I = 0$$

$$\therefore P_{R5} = (I_{R5})^2 (R5) = \underline{0W}$$

$$P_{R5} = \frac{(22V)^2}{3300\Omega}$$

$$= \underline{146.7mW}$$


6. See Figure 2. Which one of the following statements is true if the 120V source is replaced by a 60V source?

a. The power dissipated by R5 will decrease to half of its original value  $\times$   
b. The current in the circuit will reduce to half its original value  $\leftarrow I = V/R$   
c. The power dissipated by R5 will decrease by 25%  $\times$   
d. The voltage across R3 will decrease by 25%  $\times \leftarrow V_{R3}$  would decrease 50%.

$$P_{R5}^{NEW} = \frac{V_{R5}^2}{R5} = \frac{(11V)^2}{3300\Omega} = 36.7mW, \quad \underline{25\% \text{ of } P_{R5} \text{ original}}$$

7. The total *resistance* of a 10 ohm resistor and a 100 ohm resistor in parallel is


a. 0.110 Ohms  
 b. 7.07 Ohms  
 c. 9.09 Ohms  
 d. 1010 Ohms



$$R_T = \frac{10(100)}{10+100} = \underline{9.09\Omega}$$

8. A 10 ohm resistor and an 8 ohm resistor are connected in parallel across a 15 V battery. What is the total current drawn from the battery?

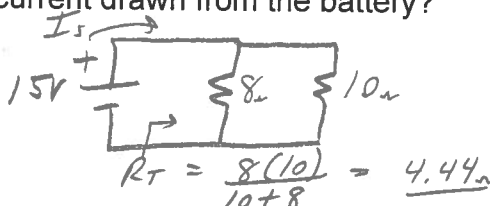a. 0.830 A  
 b. 1.50 A  
 c. 1.88 A  
 d. 3.38 A



$$I_s = \frac{15V}{R_T} = \frac{15V}{4.44\Omega} = \underline{3.38A}$$

9. What is the total conductance of a parallel circuit with three resistors with values of 80, 120 and 220 ohms?

a. 25.4 mS  
 b. 39.4 mS  
 c. 53.8 mS  
 d. 39.4 S

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{1}{\frac{1}{80} + \frac{1}{120} + \frac{1}{220}} = \underline{39.4\Omega}$$

$$\therefore G_T = \frac{1}{R_T} = \underline{25.4mS}$$

$$\text{or } G_T = \frac{1}{80\Omega} + \frac{1}{120\Omega} + \frac{1}{220\Omega} = \underline{25.4mS}$$

10. As additional resistors are added (in parallel) to a parallel circuit, what will happen to the total conductance of the circuit?

a. The total conductance will decrease  
 b. The total conductance will increase  
 c. The total conductance will remain the same  $\times$   
 d. It depends on the number of resistors added whether the conductance will increase or decrease  $\times$

$$R_T \downarrow \therefore G_T \uparrow$$

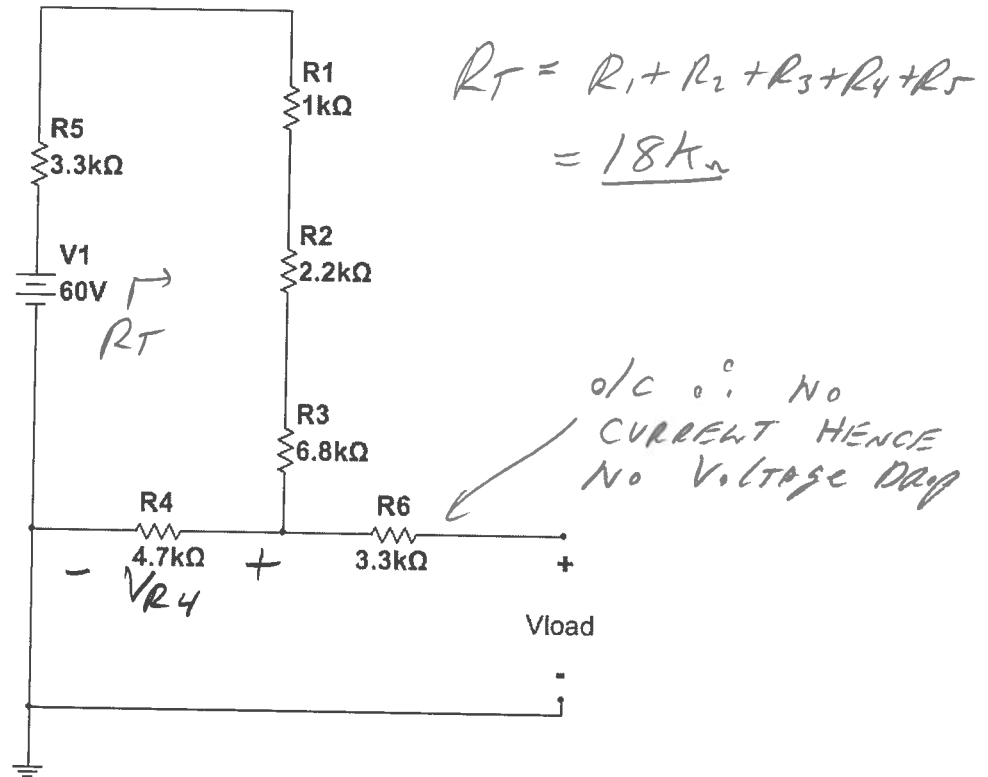


Figure 3 - Schematic for Questions 11, 12 and 13

11. See Figure 3. What is the open circuit output voltage  $V_{load}$ ?

a. 0 V  
 b. 15.7 V  
 c. 21.2 V  
 d. 60 V

$$V_{R4} = V_1 \left( \frac{R_4}{R_T} \right) = 60V \left( \frac{4700\Omega}{18k\Omega} \right) = 15.67V$$

KVL:  $V_{R4} - V_{R6} - V_{LOAD} = 0$   
 $\therefore V_{LOAD} = V_{R4}$

12. See Figure 3. What is the new voltage  $V_{load}$  if  $R_4$  is shorted?

a. 0 V  
 b. 14.9 V  
 c. 21.2 V  
 d. 60 V

$$V_{LOAD} = V_{R4} = 0V$$

13. See Figure 3. What is the new voltage  $V_{load}$  if  $R_4$  is open-circuited?

a. 0 V  
 b. 14.9 V  
 c. 21.2 V  
 d. 60 V

$$V_{R4} = V_1 = 60V \quad (\because \text{No current} \therefore \text{No voltage drop})$$

$\therefore V_{LOAD} = 60V$

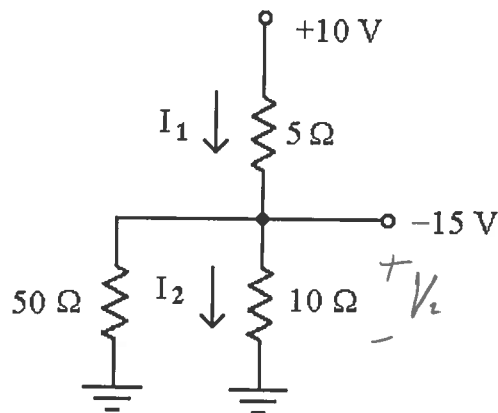


Figure 7.6

14. See Figure 7.6. What is the current  $I_2$ ?

a. -2.0 A  
 b. -1.5 A  
 c. 1.5 A  
 d. 5.0 A

$$I_2 = \frac{V_2}{10\Omega} = \frac{-15V}{10\Omega} = \underline{\underline{-1.5A}}$$

15. See Figure 7.6. What is the power dissipated by the 50 ohm resistor?

a. 1.5 W  
 b. 2.0 W  
 c. 4.5 W  
 d. 22.5 W

$$P_{50\Omega} = \frac{(V_2)^2}{50\Omega} = \frac{(-15V)^2}{50\Omega} = \underline{\underline{4.5W}}$$

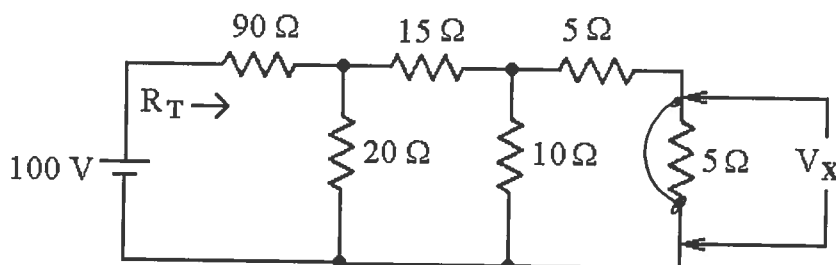


Figure 7.5

16. See Figure 7.5. What is  $R_T$  if the 5 ohm resistor on the far right is short-circuited?

a. 18.7 Ohms  
 b. 90.0 Ohms  
 c. 99.6 Ohms  
 d. 110 Ohms

$$R_T = ([5\Omega // 10\Omega] + 15\Omega) // 20\Omega + 90\Omega$$

$$18.33\Omega // 20\Omega + 90\Omega$$

$$\underline{\underline{R_T = 99.6\Omega}}$$

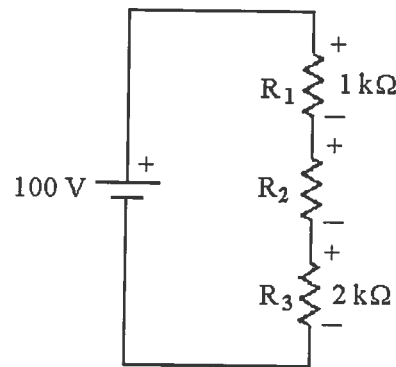


Figure 5.6

17. See Figure 5.6. Use voltage divider to choose  $R_2$  such that  $V_{R3} = 30\text{ V}$  (polarity as shown)

$$V_{R3} = 100\text{ V} \left( \frac{R_3}{R_T} \right) = 30\text{ V}, \quad R_T = R_1 + R_2 + R_3 = 3\text{ k}\Omega + R_2$$

$$\therefore 100\text{ V} \left( \frac{2\text{ k}\Omega}{R_2 + 3\text{ k}\Omega} \right) = 30\text{ V}$$

$$\boxed{R_2 = 3.67\text{ k}\Omega}$$

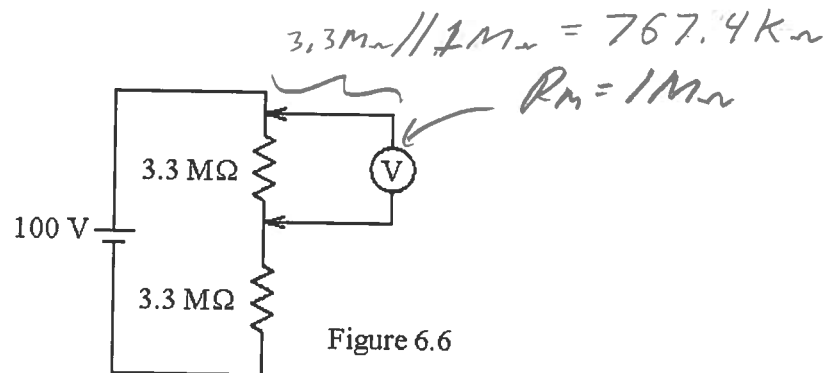


Figure 6.6

18. See Figure 6.6. Compute the voltage reading if a digital multimeter with 1 M-ohm of internal resistance is used.

$$V = 100\text{ V} \left( \frac{767.4\text{ k}\Omega}{767.4\text{ k}\Omega + 3.3\text{ M}\Omega} \right) = \boxed{18.9\text{ V}}$$


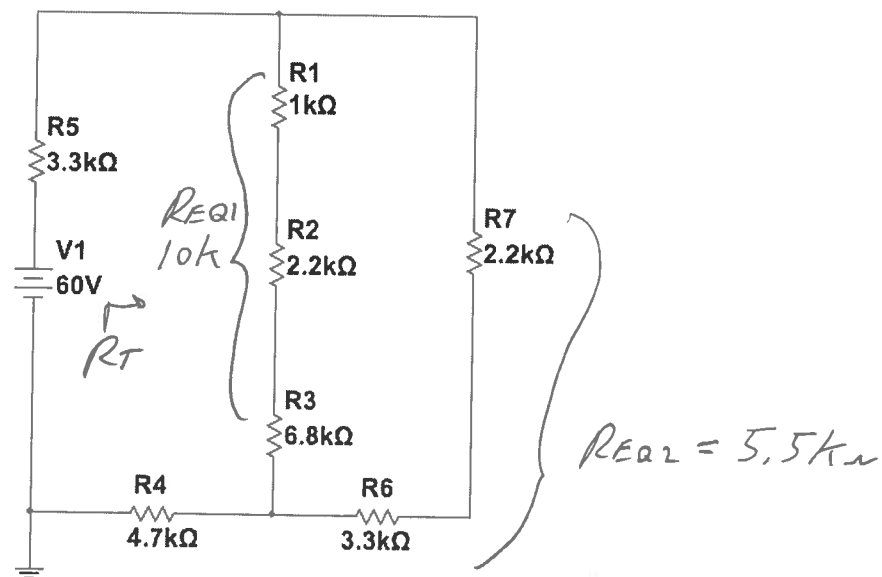


Figure 4 - Schematic for Questions 19 and 20

19. See Figure 4. What is the total resistance seen by the source?


$$R_T = \underbrace{5.5k\Omega // 10k\Omega}_{3.548k\Omega} + 3300\Omega + 4700\Omega$$

$$R_T = 11.55k\Omega$$

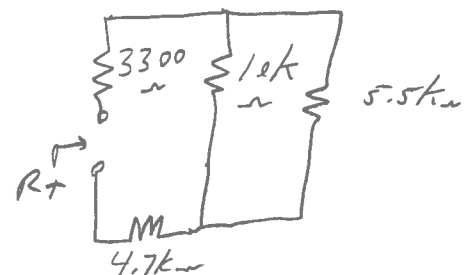

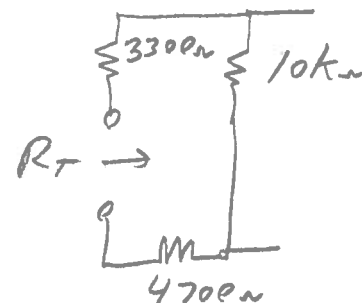20. See Figure 4. If R6 is replaced by an open-circuit, what is the total resistance seen by the source?

$$R_T = 3300\Omega + 10k\Omega + 4700\Omega = 18k\Omega$$





**KEY****1. C****2. B****3. A****4. D****5. A****6. B****7. C****8. D****9. A****10. B****11. B****12. A****13. D****14. B****15. C****16. C****17. 3,667 Ohms****18. 18.87 V****19. 11,548 Ohms****20. 18,000 Ohms**