

FULL NAME (Printed): _____

Program: _____

You have the entire period to complete this examination. You are allowed your Sharp EL-516 calculator and the DC Formula Sheet from the text (provided). All of the questions are equally weighted

- **M/C Questions**

- ☐ Circle the correct answer
- ☐ NO partial credit will be awarded

- **Work the Problem Questions**

- ☐ SHOW ALL your work in the space provided
 - ☐ BOX-IN your final answer
 - ☐ Partial credit may be awarded
-

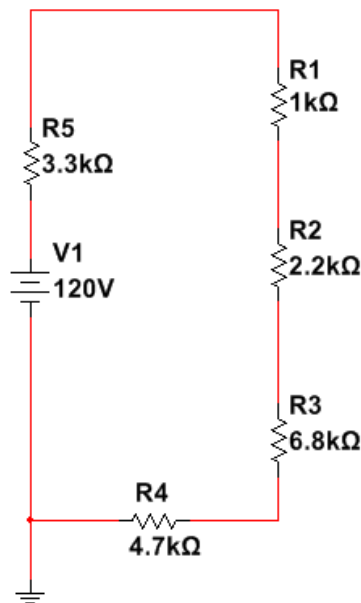


Figure 1- Schematic for Problems 1 through 3

1. See Figure 1. How much power is dissipated by R₅?
 - a. 146.7 mW
 - b. 132.2 mW
 - c. 36.4 mW
 - d. 6.67 mW

2. See Figure 1. If R₃ is open circuited, how much power is dissipated by R₅?
 - a. 36.4 mW
 - b. 6.76 mW
 - c. 1.76 mW
 - d. 0 W

3. See Figure 1. Which *one* of the following statements is true *if the 120V source is replaced by a 60V source*?
 - a. The voltage across R₃ will decrease by 25%
 - b. The power dissipated by R₅ will decrease by 25%
 - c. The current in the circuit will reduce to half its original value
 - d. The power dissipated by R₅ will decrease to half of its original value

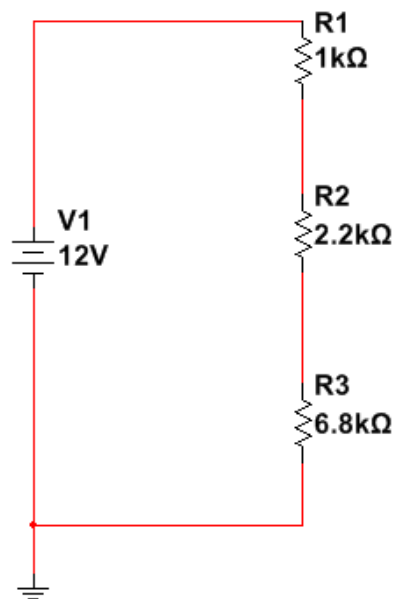


Figure 2- Schematic for Problems 4 - 6

4. See Figure 2. The total resistance in this circuit is (as seen by the source):
 - a. 12 kΩ
 - b. 10 kΩ
 - c. 1 kΩ
 - d. 0.624 kΩ

5. See Figure 2. The total current flowing from the battery is
 - a. 12 mA
 - b. 1.8 mA
 - c. 1.2 mA
 - d. 1.0 mA

6. See Figure 2. The total power dissipated by the 2.2 kΩ resistor is
 - a. 144 mW
 - b. 23.2 mW
 - c. 14.4 mW
 - d. 3.17 mW

7. The total *resistance* of a $10\ \Omega$ resistor and a $100\ \Omega$ resistor in parallel is
 - a. $1010\ \Omega$
 - b. $9.09\ \Omega$
 - c. $7.07\ \Omega$
 - d. $0.110\ \Omega$

8. A $10\ \Omega$ resistor and an $8\ \Omega$ resistor are connected in parallel across a $15\ \text{V}$ battery. What is the total current drawn from the battery?
 - a. $3.38\ \text{A}$
 - b. $1.88\ \text{A}$
 - c. $1.50\ \text{A}$
 - d. $0.830\ \text{A}$

9. What is the total conductance of a parallel circuit with three resistors with values of 80 , 120 and $220\ \Omega$?
 - a. $39.4\ \text{S}$
 - b. $53.8\ \text{mS}$
 - c. $39.4\ \text{mS}$
 - d. $25.4\ \text{mS}$

10. As additional resistors are added (in parallel) to a parallel circuit, what will happen to the total conductance of the circuit?
 - a. It depends on the number of resistors added whether the conductance will increase or decrease
 - b. The total conductance will remain the same
 - c. The total conductance will increase
 - d. The total conductance will decrease

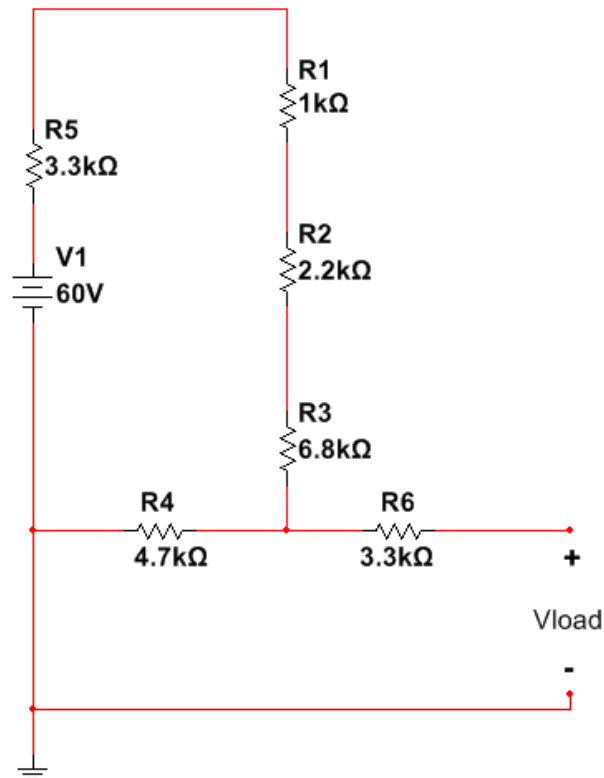


Figure 3 - Schematic for Questions 11, 12 and 13

11. See Figure 3. What is the open circuit output voltage V_{load} ?
 - a. 60 V
 - b. 21.2 V
 - c. 15.7 V
 - d. 0 V

12. See Figure 3. What is the new voltage V_{load} if R_4 is shorted?
 - a. 60 V
 - b. 21.2 V
 - c. 14.9 V
 - d. 0 V

13. See Figure 3. What is the new voltage V_{load} if R_4 is open-circuited?
 - a. 60 V
 - b. 21.2 V
 - c. 14.9 V
 - d. 0 V

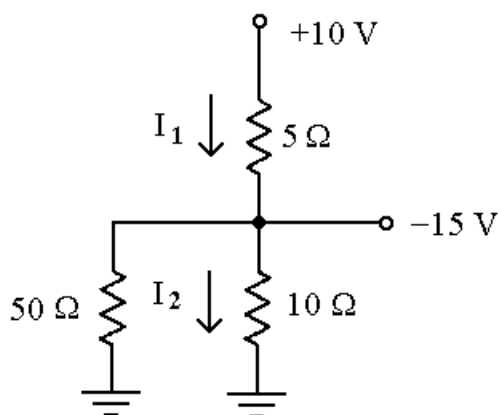


Figure 7.6

14. See Figure 7.6. What is the current I_2 ?
- 5.0 A
 - 1.5 A
 - 1.5 A
 - 2.0 A
15. See Figure 7.6. What is the power dissipated by the $50\ \Omega$ resistor?
- 22.5 W
 - 4.5 W
 - 2.0 W
 - 1.5 W

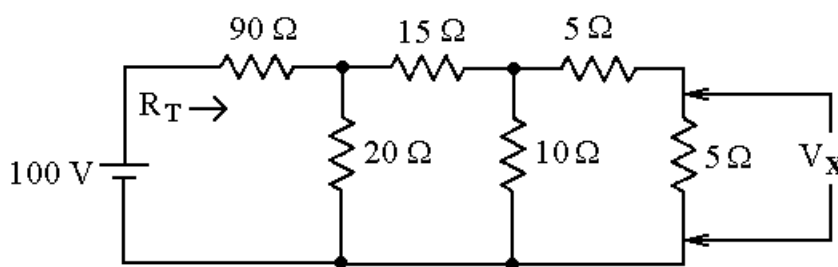


Figure 7.5

16. See Figure 7.5. What is R_T if the $5\ \Omega$ resistor on the far right is short-circuited?
- 110 Ω
 - 99.6 Ω
 - 90.0 Ω
 - 18.7 Ω

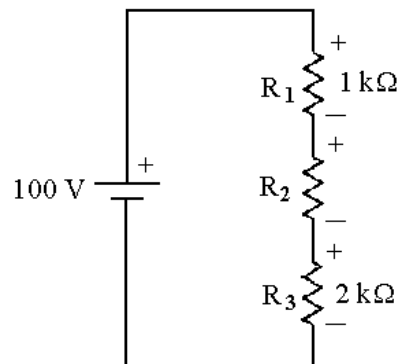


Figure 5.6

17. See Figure 5.6. Use voltage divider to choose R_2 such that $V_{R3} = 30\text{ V}$ (polarity as shown)

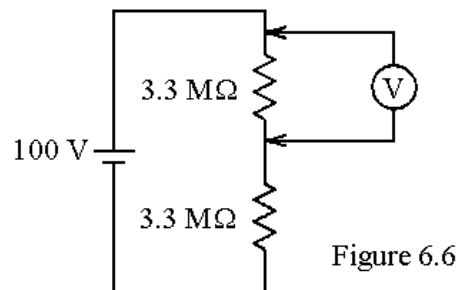


Figure 6.6

18. See Figure 6.6. Compute the voltage reading if a digital multimeter with $1\text{ M}\Omega$ of internal resistance is used.

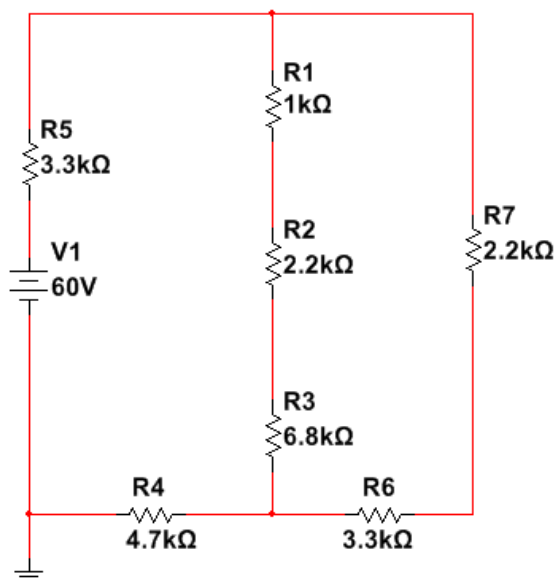


Figure 4 - Schematic for Questions 19 and 20

19. See Figure 4. What is the total resistance seen by the source?

20. See Figure 4. If R6 is replaced by an open-circuit, what is the total resistance seen by the source?

dc

Introduction

Conversions 1 meter = 100 cm = 39.37 in., 1 in. = 2.54 cm,
1 yd = 0.914 m = 3 ft, 1 mile = 5280 ft, °F = 9/5°C + 32, °C =
5/9(°F - 32), K = 273.15 + °C **Scientific notation** 10^{12} =
tera = T, 10^9 = giga = G, 10^6 = mega = M, 10^3 = kilo = k, 10^{-3} =
milli = m, 10^{-6} = micro = μ , 10^{-9} = nano = n, 10^{-12} = pico = p
Powers of ten $1/10^n = 10^{-n}$, $1/10^{-n} = 10^n$, $(10^n)(10^m) = 10^{n+m}$,
 $10^n/10^m = 10^{n-m}$, $(10^n)^m = 10^{nm}$

Voltage and Current

Coulomb's law $F = kQ_1Q_2/r^2$, $k = 9 \times 10^9 \text{ N} \cdot \text{m}^2/\text{C}^2$,
 Q = coulombs (C), r = meters (m) **Current** $I = Q/t$ (amperes),
 t = seconds (s), $Q_e = 1.6 \times 10^{-19} \text{ C}$ **Voltage** $V = W/Q$ (volts),
 W = joules (J)

Resistance

Circular wire $R = \rho l/A$ (ohms), ρ = resistivity, l = feet,
 $A_{\text{CM}} = (d_{\text{mils}})^2$, $\rho(\text{Cu}) = 10.37$ **Metric units** l = cm, A = cm^2 ,
 $\rho(\text{Cu}) = 1.724 \times 10^{-6} \text{ ohm-cm}$ **Temperature** $(|T_i| + T_1)/R_1 =$
 $(|T_i| + T_2)/R_2$, $R_1 = R_{20}[1 + \alpha_{20}(T_1 - 20^\circ\text{C})]$, $\alpha_{20}(\text{Cu}) = 0.00393$
Color code Bands 1-3: 0 = black, 1 = brown, 2 = red, 3 = orange,
4 = yellow, 5 = green, 6 = blue, 7 = violet, 8 = gray, 9 = white,
Band 3: 0.1 = gold, 0.01 = silver, Band 4: 5% = gold, 10% = silver,
20% = no band, Band 5: 1% = brown, 0.1% = red, 0.01% = orange,
0.001% = yellow **Conductance** $G = 1/R$ siemens (S)

Ohm's Law, Power, and Energy

Ohm's law $I = E/R$, $E = IR$, $R = E/I$ **Power** $P = W/t =$
 $VI = I^2R = V^2/R$ (watts), 1 hp = 746 W
Efficiency $\eta\% = (P_o/P_i) \times 100\%$, $\eta_T = \eta_1 \cdot \eta_2 \cdot \eta_3 \cdots \eta_n$
Energy $W = Pt$, $W(\text{kWh}) = [P(\text{W}) \cdot t(\text{h})]/1000$

Series Circuits

$R_T = R_1 + R_2 + R_3 + \cdots + R_N$, $R_T = NR$, $I = E/R_T$, $V = IR$
Kirchhoff's voltage law $\sum_{\text{c}} V = 0$, $\sum_{\text{c}} V_{\text{rises}} = \sum_{\text{c}} V_{\text{drops}}$
Voltage divider rule $V_x = R_x E/R_T$

Parallel dc Circuits

$R_T = 1/(1/R_1 + 1/R_2 + 1/R_3 + \cdots + 1/R_N)$, $R_T = R/N$,
 $R_T = R_1 R_2 / (R_1 + R_2)$, $I = EG_T = E/R_T$
Kirchhoff's current law $\sum I_{\text{entering}} = \sum I_{\text{leaving}}$
Current divider rule $I_x = (R_T/R_x)I$, (Two parallel elements):
 $I_1 = R_2 I / (R_1 + R_2)$, $I_2 = R_1 I / (R_1 + R_2)$

Series-Parallel Circuits

Potentiometer loading $R_L \gg R_T$
Ammeter $R_{\text{shunt}} = R_m I_{\text{CS}} / (I_{\text{max}} - I_{\text{CS}})$
Voltmeter $R_{\text{series}} = (V_{\text{max}} - V_{\text{VS}}) / I_{\text{CS}}$
Ohmmeter $R_s = (E/I_{\text{CS}}) - R_m - \text{zero-adjust}/2$

Methods of Analysis and Selected Topics (dc)

Source conversions $E = IR_p$, $R_s = R_p$, $I = E/R_s$

Determinants $D = \begin{vmatrix} a_1 & b_1 \\ a_2 & b_2 \end{vmatrix} = a_1 b_2 - a_2 b_1$

Bridge networks $R_1/R_3 = R_2/R_4$ **Δ -Y conversions** $R' =$
 $R_A + R_B + R_C$, $R_3 = R_A R_B / R'$, $R_2 = R_A R_C / R'$, $R_1 = R_B R_C / R'$, $R_Y = R_{\Delta}/3$
Y- Δ conversions $R' = R_1 R_2 + R_1 R_3 + R_2 R_3$, $R_C = R' / R_3$, $R_B = R' / R_2$,
 $R_A = R' / R_1$, $R_{\Delta} = 3R_Y$

Network Theorems

Superposition Voltage sources (short-circuit equivalent), current
sources (open-circuit equivalent)
Thévenin's Theorem R_{Th} : (all sources to zero), E_{Th} : (open-circuit
terminal voltage)
Maximum power transfer theorem $R_L = R_{Th} = R_N$, $P_{\text{max}} =$
 $E_{Th}^2 / 4R_{Th} = I_{N}^2 R_N / 4$

Capacitors

Capacitance $C = Q/V = \epsilon A/d = 8.85 \times 10^{-12} \epsilon_r A/d$ farads (F),
 $C = \epsilon_r C_o$ **Electric field strength** $\mathcal{E} = V/d = Q/\epsilon A$ (volts/meter)
Transients (charging) $i_C = (E/R)e^{-t/\tau}$, $\tau = RC$, $v_C = E(1 - e^{-t/\tau})$,
(discharge) $v_C = Ee^{-t/\tau}$, $i_C = (E/R)e^{-t/\tau}$ i_C $i_{C_{\text{av}}} = C(\Delta v_C / \Delta t)$
Series $Q_T = Q_1 = Q_2 = Q_3$, $1/C_T = (1/C_1) + (1/C_2) + (1/C_3) + \cdots +$
 $(1/C_N)$, $C_T = C_1 C_2 / (C_1 + C_2)$ **Parallel** $Q_T = Q_1 + Q_2 + Q_3$,
 $C_T = C_1 + C_2 + C_3$ **Energy** $W_C = (1/2)CV^2$

Inductors

Self-inductance $L = N^2 \mu A / l$ (henries), $L = \mu_r L_o$
Induced voltage $e_{L_{\text{av}}} = L(\Delta i / \Delta t)$ **Transients** (storage) $i_L =$
 $I_m(1 - e^{-t/\tau})$, $I_m = E/R$, $\tau = L/R$, $v_L = Ee^{-t/\tau}$ (decay), $v_L =$
 $[1 + (R_2/R_1)]Ee^{-t/\tau'}$, $\tau' = L/(R_1 + R_2)$, $i_L = I_m e^{-t/\tau}$, $I_m = E/R_1$
Series $L_T = L_1 + L_2 + L_3 + \cdots + L_N$ **Parallel** $1/L_T = (1/L_1) +$
 $(1/L_2) + (1/L_3) + \cdots + (1/L_N)$, $L_T = L_1 L_2 / (L_1 + L_2)$
Energy $W_L = 1/2(LI^2)$

Magnetic Circuits

Flux density $B = \Phi/A$ (webers/m²) **Permeability** $\mu = \mu_r \mu_o$ (Wb/A · m)
Reluctance $\mathcal{R} = l/\mu A$ (rels) **Ohm's law** $\Phi = \mathcal{F}/\mathcal{R}$ (webers)
Magnetomotive force $\mathcal{F} = NI$ (ampere-turns) **Magnetizing**
force $H = \mathcal{F}/l = NI/l$ **Ampère's circuital law** $\sum_{\text{c}} \mathcal{F} = 0$
Flux $\sum \Phi_{\text{entering}} = \sum \Phi_{\text{leaving}}$ **Air gap** $H_g = 7.96 \times 10^5 B_g$

Greek Alphabet

Letter	Capital	Lowercase	Letter	Capital	Lowercase
Alpha	A	α	Nu	N	ν
Beta	B	β	Xi	Ξ	ξ
Gamma	Γ	γ	Omicron	O	o
Delta	Δ	δ	Pi	Π	π
Epsilon	E	ϵ	Rho	P	ρ
Zeta	Z	ζ	Sigma	Σ	σ
Eta	H	η	Tau	T	τ
Theta	Θ	θ	Upsilon	Υ	υ
Iota	I	ι	Phi	Φ	ϕ
Kappa	K	κ	Chi	X	χ
Lambda	Λ	λ	Psi	Ψ	ψ
Mu	M	μ	Omega	Ω	ω

Prefixes

Multiplication Factors	SI Prefix	SI Symbol
1 000 000 000 000 000 000 = 10^{18}	exa	E
1 000 000 000 000 000 = 10^{15}	peta	P
1 000 000 000 000 = 10^{12}	tera	T
1 000 000 000 = 10^9	giga	G
1 000 000 = 10^6	mega	M
1 000 = 10^3	kilo	k
0.001 = 10^{-3}	milli	m
0.000 001 = 10^{-6}	micro	μ
0.000 000 001 = 10^{-9}	nano	n
0.000 000 000 001 = 10^{-12}	pico	p
0.000 000 000 000 001 = 10^{-15}	femto	f
0.000 000 000 000 000 001 = 10^{-18}	atto	a